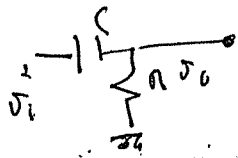


1.2) Pm 12.

RESOLUTION EXERCISE 5-7-2005

1.2)  $\frac{V_o}{V_i} : \frac{1}{2nRC} = f_c \Rightarrow C = 0.1 \mu F$

$f_c = 50 \text{ Hz}$

$R = 2n50$

$RC = \frac{1}{2n50}$

$R = \frac{1}{2n50 \cdot 0.1 \cdot 10^{-6}} = 3183 \text{ K} \rightarrow 33 \text{ K}$

1.2) $R_2 = 220 \text{ K}$

3.2) $R_{comp} = R_1 || R_2 = 9179 \text{ K} \approx 10 \text{ K}$


$\frac{1}{2nRC} = 100 \text{ Hz} : C = \frac{1}{2n \cdot 9179 \cdot 100} = 0.162 \mu F \rightarrow 162 \text{ nF}$

4.2) $R_1 = 1 \text{ K}$ $R_2 = 100 \text{ K}$ $R = 1 \text{ K}$

$\frac{1}{2nR \cdot C} = f_{BL} \Rightarrow f_{BL} = \frac{1}{2n \cdot 10^3 \cdot 0.1 \cdot 10^{-6}} = 1.591 \text{ Hz}$

5.2) $f_z = A_{OLC} \cdot f_{BLC} \Rightarrow f_{OLC} = \frac{1 \text{ MHz}}{100} = 10 \text{ KHz}$

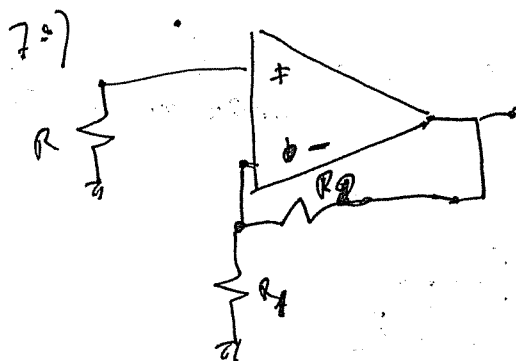6.2) $A_{OLC} = -R_2/R_1 = 47$
 $f_{OLC} = \frac{1 \text{ MHz}}{47} = 21300 \text{ Hz}$



$V^+ = -R I_{B111}$

$V^- = -(R_1 || R_2) I_{B111} + \frac{R_1}{R_1 + R_2} V_o$

$-(R_1 || R_2) I_{B111} + \frac{R_1}{R_1 + R_2} V_o = -R I_{B111}$

$\left[\frac{R_1 R_2}{R_1 + R_2} + R \right] I_{B111} = \frac{R_1}{R_1 + R_2} V_o$


$V_o = \left(\frac{R_1 R_2}{R_1} + \frac{R(R_1 + R_2)}{R_1} \right) I_{B111}$

$V_o = \left[R_2 + R \left(1 + \frac{R_2}{R_1} \right) \right] I_{B111} = 470 \text{ K} + 1 \text{ K} (1 + 47) \cdot I_{B111}$

Si $I_{B111} = 100 \text{ nA} \Rightarrow V_o = 51.8 \text{ mV}$

$518 \text{ K} I_{B111}$

8:)

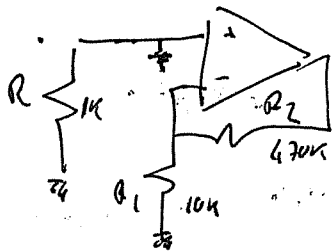

$$V^-(G_1 + G_2) - G_2 V_U = 0$$

$$V = V_{OFFIN}$$


$$V_m = \frac{G_1 + G_2}{G_2} = \left(1 + \frac{R_2}{R_1}\right) V_{OFFIN}$$

$$V_{OFFIN} = 5mV$$

$\Rightarrow$

$$V_{OFFOUT} = 48 \times V_{OFFIN} = 48 \times 5 = \underline{\underline{240mV}}$$

9:)

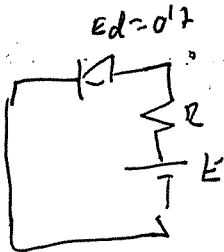

$$\frac{15 - 0.7}{R} = 5mA$$

$$R = 2.86k$$

10:)

$$r_d = \frac{V_T}{I_{DQ}} = \frac{26mV}{5mA} = 5.2\Omega$$

$$V_T = kT$$

$$T = 300^{\circ}K$$

$$V_T = 26mV$$

$$T = 360^{\circ}K$$

$$V_T = 31.2mV$$

$$V_T = 31.2mV$$

11:)

$$r_d = \frac{31.2mV}{5mA} = 6.24\Omega$$

12:)

$$f_c = 1kHz$$

$$\frac{1}{2\pi R_2 C_1} = 1kHz \Rightarrow$$


$$C_1 = \frac{1}{2\pi \times 10^3 \times 100}$$

$$C_1 = 796pF$$

$$C_1 = 796pF$$

13:)

$$1\mu F$$

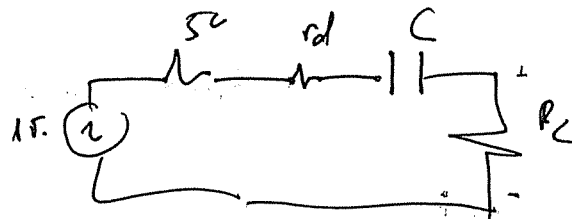


$$I_{DQ} = \frac{15 - 0.7}{R_2} \approx 100\mu A \Rightarrow$$

$$R_2 = 150k \Rightarrow$$

$$\frac{V_o}{V_i} = \frac{R_2 C s}{1 + (R_2 + r_d) C s}$$
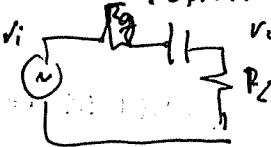
$$r_d = \frac{31.2mV}{100\mu A} = 312\Omega$$



$$V_o = \frac{R_2}{R_2 + r_d + \frac{1}{Cs}} V_i =$$

$$\frac{R_2 C s}{1 + Cs(R_2 + r_d)}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{R_2 C \omega}{\sqrt{1 + (R_2 + r_d)^2 C^2 \omega^2}}$$

$$\omega = 2\pi f$$

$$2\pi \times 5000 \times 10^{-6}$$

$$\sqrt{1 + (2\pi \times 5000)^2 \times (10^{-6})^2 \times (100)^2}$$

$$a_{fc} = \frac{1}{2\pi(R_2 + R_3)C} = 1591$$

$$= \frac{2\pi \times 1000 \times 10^{-6}}{100}$$

$$\frac{R_2 C \omega}{\sqrt{1 + ((R_2 + R_3) C \omega)^2}} = \frac{50 \times 10^{-6} \times 2\pi \times 1000}{1.395}$$

$$= \frac{0.314}{1.395} = 0.225 \times 1$$

$$\Rightarrow V_c = 225 \text{ mV}$$

$$\frac{R_2 C \omega}{\left(\frac{1}{(R_2 + R_3)k}\right)}$$

@ 20 kHz estans a una funció per respondre a la de caràcter per tant $V_c = \frac{R_3 + R_2}{R_c + R_g} = 0.5 \times 100 \text{ mV} = 50 \text{ mV}$

a) 1.551 kHz es pressiona la funció respondre a la de caràcter

per tant: $V_c = 0.5 - 0.2 \text{ V} = 0.5 - 0.7 \times 100 \text{ mV} = 35 \text{ mV}$



$$\textcircled{1} 1 \text{ kHz } L \omega$$

$$\frac{V}{Z_2} \leq 0.05 \times \frac{V}{50}$$

$$Z_2 \geq \frac{50}{0.05} = 1 \text{ k}\Omega$$


$$1 \text{ k} = L = 2\pi f$$

$$L = \frac{1.000}{2\pi \times 1000} = 159.1 \text{ mH}$$

Figura 2. Transistorul cu siliciu, BJT $\beta_{min} = 50$ // $\beta_{max} = 150$ // $\angle$

Si $R_2 = 33 \Omega$. Calculați valoarea minimă a R_1 pentru a garanta că pentru orice valoare a temperaturii, tranzistorul va funcționa în regiunea de activare.

$$V_1 = 6,0 \text{ V}$$

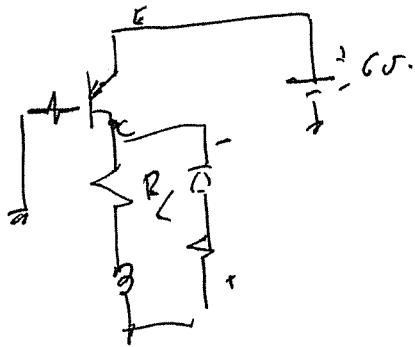

$$I_C = \frac{6 - 0.2}{R_2} = \frac{6 - 0.2}{33} = 175.75 \mu A$$

$$I_B > \frac{I_C}{\beta_{min}} = \frac{175.75}{50} = 3.515 \mu A$$

$$\frac{6 - 0.8}{R_1} = 3.515 \mu A \Rightarrow R = \underline{\underline{1.47 k\Omega}}$$

$$V_{CE} = 0.1 \text{ V}$$

$$\frac{6 - 0.8}{4.7 k} = 1.1 \mu A$$

$$3.5 \mu A = \frac{6 - 0.2}{R} \Rightarrow$$

$$R_{min} = 1.47 k\Omega$$

$$\frac{\angle}{R} = \frac{100}{320}$$

$$\frac{\angle}{R_1 + R_2} =$$

$$\frac{1 \mu A}{320} =$$

$$\frac{0.1}{320}$$

$$R_2 + R_3$$